 
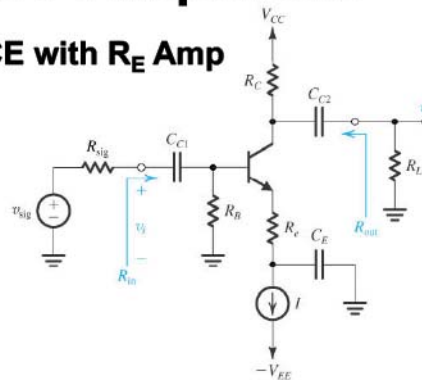
 
 



## Outline

- Device Structure and Physical Operation
  - Current-Voltage Characteristics
- The BJT as an Amplifier
  - Biasing in BJT Amplifier Circuits
  - Small-Signal Operation and Models
- Single-Stage BJT Amplifiers
  - ➔ **Design Of Single-Stage BJT Amplifiers**
    - Simulating BJT Circuits With SPICE
    - CE Amplifier Example
- Frequency Response Behavior
  - CE Amplifier
- Summary


## Single Stage BJT Amplifiers

**CE Amp**

**CE with  $R_E$  Amp**

 **CB Amp**

**CC Amp**

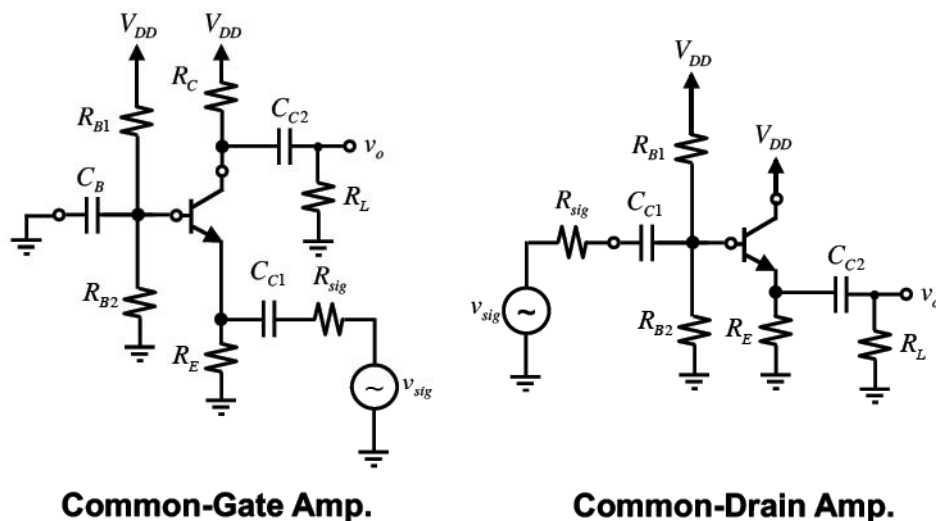
## Single-Power Supply Common-Source Amplifier With Resistor Biasing



## Discrete Implementation Of Single-Supply CMOS Amplifiers



Common-Gate Amp.

Common-Drain Amp.

## Basic BJT Amplifier Attributes

Amplifier	No-Load Voltage Gain	Current Gain	Input Resistance	Output Resistance
CE	No greater than 300 V/V (-ve)	$\beta$	Large (10k – 100k)	High (10k – 100k)
CB	No greater than 300 V/V (+ve)	$\alpha$	Small (10 – 10k)	High (10k – 100k)
CC	Near Unity +ve	$\beta+1$	Medium (1k – 10k)	Small (10 – 1k)

## Design Of A CE Amplifier


The design problem is to select  $V_E$ ,  $V_C$  and  $I_C$ .

$V_B$  is not a design variable, as it can be expressed as

$$V_B = V_E + V_T \ln(I_C/I_S) \approx V_E + 0.7 \text{ V}$$

Another design variable is  $R_{B1}$ . We are free to choose any value for it to set  $V_B$ :
 
$$V_B = \frac{R_{B2}}{R_{B1} + R_{B2}} V_{CC} \Rightarrow R_{B2} = \left( \frac{V_B}{V_{CC} - V_B} \right) R_{B1}$$



## Design Of A CE Amplifier Biasing Considerations

There are several biasing constraints on BJT amps:

- (1) The input resistance to the amplifier should be set much larger than the source resistance to reduce any signal loss, i.e.,


$$R_{in} = R_{B1} \parallel R_{B2} \parallel ((\beta+1)r_e) \gg R_{sig} \Rightarrow R_{B1} \parallel R_{B2} \parallel \frac{(\beta+1)V_T}{I_C} \gg R_{sig}$$

**Condition is not critical as the gain loss can be corrected using the transistor gain.**

- (2) Bias current through resistor divider at base terminal  $V_{DD}/(R_{B1}+R_{B2})$  must be much greater than the transistor base current  $I_C/(\beta+1)$ , i.e.

$$\frac{V_{CC}}{R_{B1}+R_{B2}} \gg \frac{I_C}{(\beta+1)} \Rightarrow \frac{(V_E+0.7)(\beta+1)}{I_C} \gg R_{B1}$$

 **$R_{B1}$  should be made small enough to ensure voltage divider current is much greater than transistor base current.**



## Design Of A CE Amplifier Biasing Considerations

- (3) The collector current  $I_C$  is selected to ensure the gain requirements are met:

Consider the loaded voltage gain of amplifier from base terminal to output terminal:

$$|A_v| = \frac{v_o}{v_b} = g_m \times R_C \parallel R_L \parallel r_o \approx |A_v^D|$$


Substituting for known values, we write

$$|A_v| = \frac{V_T}{I_C} \times \left( \frac{V_{CC}-V_C}{I_C} \parallel R_L \parallel \frac{V_A}{I_C} \right) \geq |A_v^D| \Rightarrow \frac{I_C/V_T}{\frac{I_C}{V_{CC}-V_C} + \frac{1}{R_L} + \frac{I_C}{V_A}} \geq |A_v^D|$$


After some re-arranging,

$$I_C \geq \frac{|A_v^D| \left[ \frac{1}{V_T} - \frac{|A_v^D|}{V_{CC}-V_C} - \frac{|A_v^D|}{V_A} \right]^{-1}}{R_L}$$

 **The higher the desired voltage gain, the larger the collector current.**


 
## Design Of A CE Amplifier Voltage Gain Vs. $I_C$



## Design Of A CE Amplifier Maximum Voltage Gain

We recognize from the collector current – voltage gain equation, i.e.,

$$I_C \approx \frac{|A_v^D|}{R_L} \left[ \frac{1}{V_T} - \frac{|A_v^D|}{V_{CC} - V_C} - \frac{|A_v^D|}{V_A} \right]^{-1}$$


that the denominator goes to zero when

$$\frac{1}{V_T} = \frac{|A_v^D|}{V_{CC} - V_C} + \frac{|A_v^D|}{V_A}$$


This in turn sets the upper limit on the desired voltage gain achievable by the CE amplifier as:

$$|A_{v,MAX}^D| = \left( \frac{V_T}{V_{CC} - V_C} + \frac{V_T}{V_A} \right)^{-1}$$

 
Don't expect to get more gain than above!


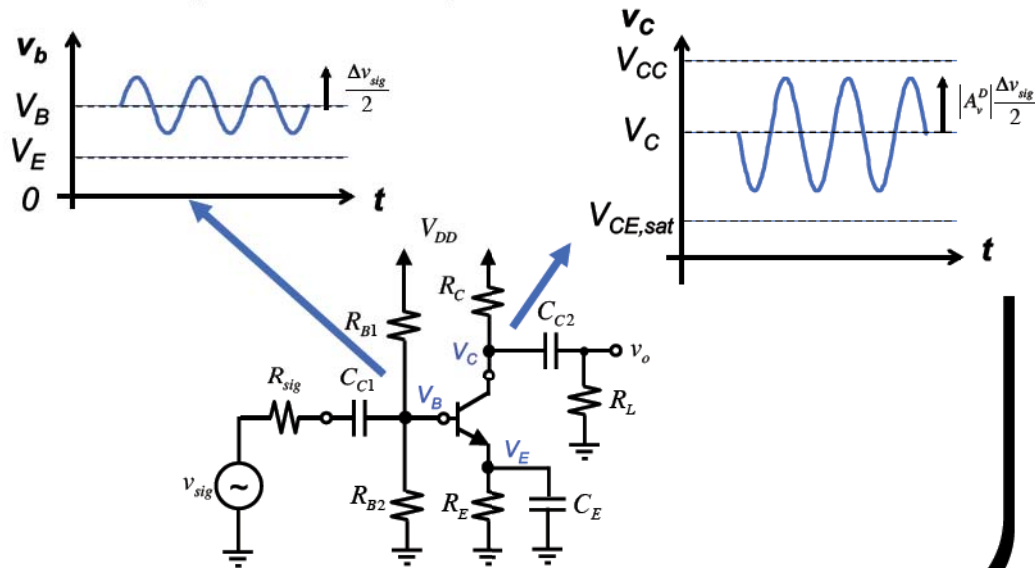
## Design Of A CE Amplifier Input and Output Signal Swings



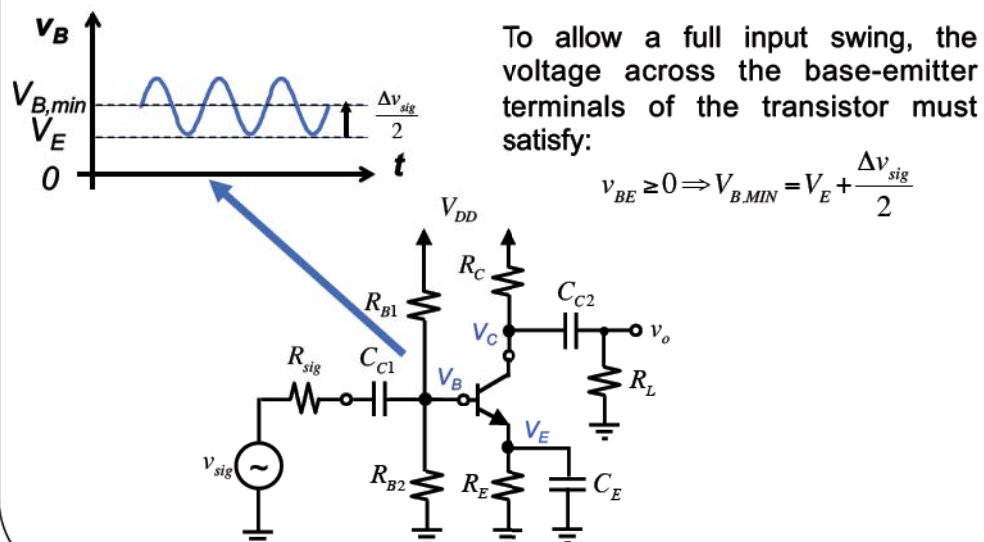
## Design Of A CE Amplifier Minimum Input Biasing Condition




 
## Design Of A CE Amplifier Maximum Output Signal Swing



© 2012 G. W. Roberts

BJT Circuits, slide 81


## Bias Levels For CE Amplifier

### Design Conditions

$$R_{in} = R_{B1} \parallel R_{B2} \parallel (\beta + 1)r_e \gg R_{sig}$$

$$\frac{V_{CC}}{R_{B1} + R_{B2}} \gg \frac{I_C}{(\beta + 1)}$$

$$|A_v^D| < \left( \frac{V_T}{V_{CC} - V_C} + \frac{V_T}{V_A} \right)^{-1}$$

 

Amplifier Type		Node Voltages				Collector Current	
		$V_E$	$V_B$	$V_{C,MIN,AC}$	$V_{C,MAX,AC}$	$I_{C,MIN}$	$I_{C,Av}$
CE	Bias Voltage	$V_E$	$V_E + V_T \ln(I_C/I_S) \approx V_E + 0.7 \text{ V}$	$V_E + V_{CE,sat} +  A_v^D  \frac{\Delta v_{sig}}{2}$	$V_{CC} -  A_v^D  \frac{\Delta v_{sig}}{2}$	$I_S e^{\left(\frac{V_E}{V_T}\right) / V_T}$	$\frac{ A_v^D }{R_L} \left[ \frac{1}{V_T} - \frac{ A_v^D }{V_{CC} - V_C} - \frac{ A_v^D }{V_A} \right]^{-1}$
	Res.	$R_{B1} = R_{nom}$		$R_{B2} = \left( \frac{V_B}{V_{CC} - V_B} \right) R_{B1}$		$R_E = \frac{V_E}{I_C}$	$R_C = \frac{V_{CC} - V_C}{I_C}$
	Caps.	$C_{C1} = \frac{1}{(R_{sig} + R_{B1} \parallel R_{B2}) \omega_{p2}}$		$C_{C2} = \frac{1}{(R_C + R_L) \omega_{p3}}$		$C_E = 1 / (R_E \parallel r_e) \omega_{p1}$	



© 2012 G. W. Roberts

BJT Circuits, slide 82

## Outline

- Device Structure and Physical Operation
  - Current-Voltage Characteristics
- The BJT as an Amplifier
  - Biasing in BJT Amplifier Circuits
  - Small-Signal Operation and Models
- Single-Stage BJT Amplifiers
- Design Of Single-Stage BJT Amplifiers
  - ➡ Simulating BJT Circuits With SPICE
    - CE Amplifier Example
- Frequency Response Behavior
  - CE Amplifier
- Summary

## SPICE BJT Statement

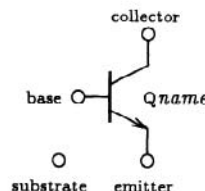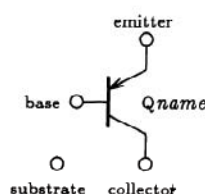Element	Spice Description
 <p>Diagram of an NPN BJT symbol. The base is on the left, collector is at the top, and emitter is at the bottom. A substrate connection is shown on the left. The emitter has an arrow pointing outwards. The label 'Qname' is next to the collector terminal.</p>	<pre>Qname collector base emitter [ substrate ] BJT_model_name [ #_in_parallel ] .MODEL BJT_model_name NPN ( parameter_name=value .... )</pre>
 <p>Diagram of a PNP BJT symbol. The base is on the left, emitter is at the top, and collector is at the bottom. A substrate connection is shown on the left. The emitter has an arrow pointing inwards. The label 'Qname' is next to the collector terminal.</p>	<pre>Qname collector base emitter [ substrate ] BJT_model_name [ #_in_parallel ] .MODEL BJT_model_name PNP ( parameter_name=value .... )</pre>

- SPICE has a built-in model for an npn and pnp BJTs.




## BJT SPICE Model


- The following is a partial listing of the SPICE parameters for a static BJT model:

Symbol	SPICE Name	Model Parameter	Units	Default
$I_S$	Is	Saturation Current	Amps	$1 \times 10^{-16}$
$\beta_F$	Bf	Forward Current Gain		100
$V_{AF}$	VAf	Forward Early Voltage	Volts	$\infty$
$r_B$	Rb	Base Ohmic Resistance	Ohms	0
$r_C$	Rc	Collector Ohmic Resistance	Ohms	0
$r_E$	Re	Emitter Ohmic Resistance	Ohms	0

## SPICE Large Signal NPN BJT Model

 


symbol

 

Equivalent SPICE Circuit

- Any time an NPN BJT appears in a circuit it is replaced by the circuit model shown here.
  - Static and dynamic behavior is captured by model.

## SPICE Curve Tracer Example

 

BJT Curve Tracer Setup

Spice As A Curve Tracer: BJT I-V Characteristics

**\*\* Circuit Description \*\***

Vce 1 0 DC 0V

Ib 0 2 DC 10uA

\* device under test

Q1 1 2 0 npn\_transistor

\* transistor model statement

.model npn\_transistor NPN (Is=1.8104e-15A Bf=100  
VAf=35V)

**\*\* Analysis Requests \*\***

\* vary Vce from 0V to 10V in steps of 100mV

.DC Vce 0V +10V 100mV Ib 1u 10u 1u


**\*\* Output Requests \*\***

.plot DC I(Vce)

.end

SPICE Input Deck


## Simulation Results IC-VCE Vs IB

 

## Frequency Response Of A CE Amp
 
### PARAMETERS:

CE = 10u  
CCI = 10u  
CCO = 10u  
RC = 10K  
RB = 340K  
RE = 6K  
Rce = 130  
RL = 10K  
Rsig = 10K  
VCC = 5  
VEE = -5



## SPICE Deck

### Common-Emitter Amplifier Stage

#### \*\* Circuit Description \*\*

#### \* power supplies

Vcc 1 0 DC +10V

Vee 8 0 DC -10V

#### \* input signal

Vs 6 0 AC 10mV

Rs 5 6 10k

#### \* amplifier

C1 4 5 1GF

Rb 4 0 100k

Q1 2 4 3 Q2N3904

Rc 1 2 10k

Re 3 8 10k

C2 2 7 1GF

C3 3 0 1GF

#### \* load + ammeter

RI 7 9 10k

Vout 9 0 0

#### \* transistor model statement for the Q2N3904

.model Q2N3904 NPN (Is=14.34f Xti=3 Eg=1.11 Vaf=74.03 Bf=255.9 Ne=1.307

+ Ise=14.34f Ikf=.2847 Xtb=1.5 Br=6.092 Nc=2 Isc=0 Ikr=0 Rc=1

+ Cjc=7.306p Mjc=.3416 Vjc=.75 Fc=.5 Cje=22.01p Mje=.377 Vje=.75

+ Tr=46.91n Tf=411.1p Itf=.6 Vtf=1.7 Xtf=3 Rb=10)

#### \*\* Analysis Requests \*\*

#### \* calculate DC bias point information

.OP


.AC DEC1 1Hz 10MegHz

#### \*\* Output Requests \*\*

#### \* voltage gain Av=Vo/Vs


.PRINT AC VdB(7)

.end

 

## Simulation Results

$R_{ce}=0$  and  $R_{ce}=130\ \Omega$

 

## Outline

- Device Structure and Physical Operation
  - Current-Voltage Characteristics
- The BJT as an Amplifier
  - Biasing in BJT Amplifier Circuits
  - Small-Signal Operation and Models
- Single-Stage BJT Amplifiers
- Design Of Single-Stage BJT Amplifiers
  - Simulating BJT Circuits With SPICE
  - ➡ CE Amplifier Example
- Frequency Response Behavior
  - CE Amplifier
- Summary

## Design Of A CE Amplifier Example

Design a DC coupled CE amplifier with a voltage gain having a magnitude of at least 30 V/V driven by a source with resistance of  $1000 \Omega$  and loaded by a  $15 \text{ k}\Omega / 10 \text{ pF}$  load. The input will vary over 20 mV voltage range with a range of signals from 100 Hz to 10 kHz. The power supply is assumed to be +12 V. The BJT can be described by  $I_s = 10^{-15} \text{ A}$ ,  $\beta = 100$  and  $V_A = 100 \text{ V}$ .

**Solution:**

The design problem is to select  $V_E$ ,  $V_C$  and  $I_C$ .


Let us begin with setting the node voltages:

$$V_E = 2.0 \text{ V}, \quad V_C = 6.0 \text{ V}$$

and approximate the base voltage as

$$V_B = V_E + 0.7 = 2.7 \text{ V}$$


 
The drain voltage is positioned almost in the middle of the power supply – the best possible place for it.



## Design Of A CE Amplifier Example

$$|A_v| = \frac{I_C / V_T}{\frac{I_C}{V_{CC} - V_C} + \frac{1}{R_L} + \frac{I_C}{V_A}}$$
  
$$V_E = 2.0 \text{ V}, \quad V_B = 2.7 \text{ V}, \quad V_C = 6.0 \text{ V}$$





## Design Of A CE Amplifier


### Example Continued

Next, we compute the desired current level from the desired voltage gain equation, i.e.,

$$I_C \geq \frac{|A_v^D|}{R_L} \left[ \frac{1}{V_T} - \frac{|A_v^D|}{V_{CC} - V_C} - \frac{|A_v^D|}{V_A} \right]^{-1}$$

First, let's check to see what the maximum achievable gain is and whether our desired gain is achievable:

$$\begin{aligned} |A_{v,MAX}^D| &= \left( \frac{V_T}{V_{CC} - V_C} + \frac{V_T}{V_A} \right)^{-1} \\ &= \left( \frac{0,025}{12-6} + \frac{0,025}{100} \right)^{-1} \\ &= (0,0042 + 0,00025)^{-1} \\ &\approx (0,0042)^{-1} \\ &= 240 \frac{V}{V} \end{aligned}$$

 

**Here we see the maximum gain of 240 V/V far exceeds our gain requirements of 30 V/V.**

## Design Of A CE Amplifier

### Example Continued

Returning to the current equation, we solve

$$I_C \geq \frac{|A_v^D|}{R_L} \left[ \frac{1}{V_T} - \frac{|A_v^D|}{V_{CC} - V_C} - \frac{|A_v^D|}{V_A} \right]^{-1}$$

$$\geq \frac{30}{15} \left[ \frac{1}{25 \times 10^{-3}} - \frac{30}{12 - 6} - \frac{30}{100} \right]^{-1} \text{ mA}$$

$$\geq 0.06 \text{ mA}$$

To provide some design margin, we'll select the collector current as


$I_C = 0.1 \text{ mA},$

Now, we can compute the upper limit to  $R_{B1}$  according to

$$\frac{(V_E + 0.7)(\beta + 1)}{I_C} \gg R_{B1} \Rightarrow \frac{(2.0 + 0.7)(100 + 1)}{0.1 \text{ mA}} \gg R_{B1} \Rightarrow 2660 \text{ k}\Omega \gg R_{B1}$$

Therefore we select  $R_{B1}$  as:

$$R_{B1} = 266 \text{ k}\Omega$$

 



## Design Of A CE Amplifier Example Continued

With  $R_{B1}$  now known, we can compute the value for  $R_{B2}$  according to


$$R_{B2} = \left( \frac{V_B}{V_{CC} - V_B} \right) R_{B1} \Rightarrow R_{B2} = \left( \frac{2.7}{12 - 2.7} \right) (266 \text{ k}\Omega) = 74.8 \text{ k}\Omega$$

Note, a more accurate value for  $V_B$  can be derived but this is seldom necessary, as the component tolerances will mask any improvement.

Next, we compute  $R_E$  and  $R_C$  according to

$$R_E = \frac{V_E}{I_C} = \frac{2 \text{ V}}{0.1 \text{ mA}} = 20 \text{ k}\Omega$$
 
$$R_C = \frac{V_{CC} - V_C}{I_C} = \frac{12 - 6 \text{ V}}{0.1 \text{ mA}} = 60 \text{ k}\Omega$$



**Final Design**

## Calculate Circuit Parameters

BJT CE Amplifier Requirements							
Input Signal Swing (V)	Desired Voltage Gain (V/V)	Lower frequency (Hz)	Upper frequency (Hz)	Source Resistance (Ohms)	Load Resistance (kOhms)	Min. Input Resistance (kOhms)	Power Supply Voltage (V)
0.020	-30.0	100	10000	1000	15	10	12

BJT Transistor Process Parameters					
# Parallel	Saturation Current (fA)	Beta	VT (mV)	Early Voltage (V)	Saturation Voltage (V)
1	1.0	100	25.0	100	0.2

Transistor Node Voltages			
Computed Value	Designer Selected		
VB (V)	IC (mA)	VE (V)	VC (V)
2.633	0.1000	2.00	6.00

Everything Below This Line Is Calculated


Collector Voltage AC Signal Limits, VC	
VC,MIN (V)	VC,MAX (V)
2.50	11.7

Collector Current Limits		
IC,min (mA)	IC,Av (mA)	Av,max (V/V)
0.0	0.0576	226.4

Transistor Parameters				Performance Metrics			
Collector Current (mA)	Transconductance gm (mA/V)	Output Resistance (kOhms)	Minimum DC Collector Voltage (V)	Actual Input-Output Voltage Gain (V/V)	Expected Output Signal Swing (V)	Maximum Available Voltage Swing (V)	Actual Input Resistance (kOhms)
0.100	4.0	1000	2.20	-44.88	0.90	9.800	17.62

Circuit Components						
Resistors				Capacitors		
RB1 (kOhms)	RB2 (kOhms)	RE (kOhms)	RC (kOhms)	CC1 (uF)	CC2 (uF)	CE (uF)
266.0	74.8	20.0	60.0	0.156	2.12	64.46


## SPICE Test Setup

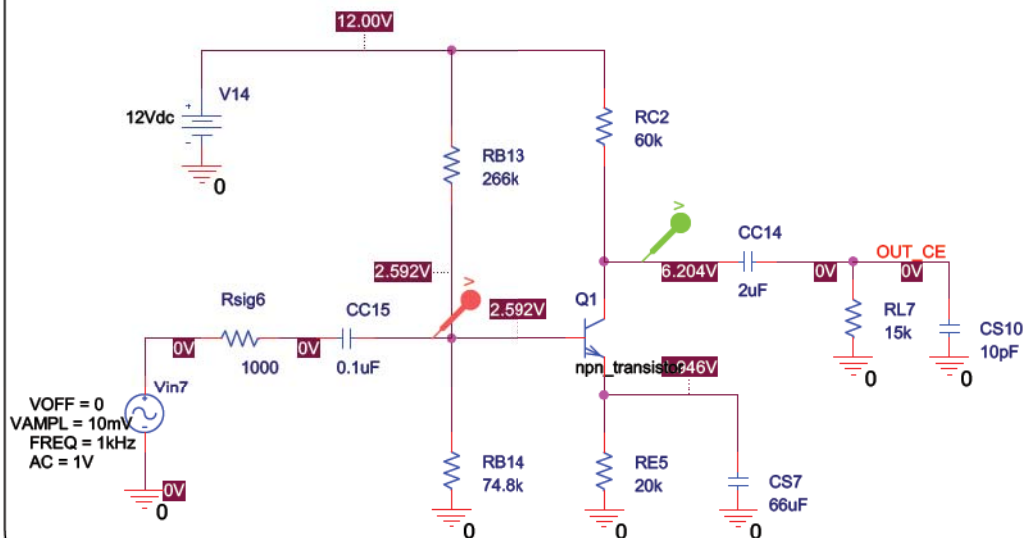


© 2012 G. W. Roberts

BJT Circuits, slide 99

## SPICE Results

 

Transient Response to 10 mV Input

 

AC Response to 1 V Input

Gain easily meets spec of -30 V/V (actual -40 V/V).


© 2012 G. W. Roberts

BJT Circuits, slide 100


## Outline

- Device Structure and Physical Operation
  - Current-Voltage Characteristics
- The BJT as an Amplifier
  - Biasing in BJT Amplifier Circuits
  - Small-Signal Operation and Models
- Single-Stage BJT Amplifiers
- Design Of Single-Stage BJT Amplifiers
  - Simulating BJT Circuits With SPICE
  - CE Amplifier Example
- ➔ Frequency Response Behavior
  - CE Amplifier
- Summary

## Attributes of a Frequency Response

 


## Hybrid-Pi BJT High-Frequency Model

 

- The hybrid-pi model is extended to higher ranges of frequencies by including the various junction capacitances and a base-spreading resistor.

## PN Junction Capacitance

 

## Capacitances

- Base-Collector Junction:**

$$C_{\mu} = \frac{C_{\mu 0}}{\left(1 + \frac{V_{CB}}{V_{0c}}\right)^m}$$


where  $C_{\mu 0}$  is the value of  $C_{\mu}$  at zero voltage,  $V_{0c}$  is the CBJ built-in voltage (typically 0.75 V) and  $m$  is its grading coefficient (typically, 0.2 – 0.5).

- Base-Emitter Junction:**

$$C_{\pi} = \frac{C_{je0}}{\left(1 - \frac{V_{BE}}{V_{0e}}\right)^m} + \tau_F \frac{I_C}{V_T} \approx 2C_{je0} + \tau_F \frac{I_C}{V_T}$$


EBJ is forward biased in the active mode, so the right most approximation is used as it is more accurate. Here  $C_{je0}$  is the value of  $C_{je}$  at zero voltage,  $\tau_F$  is the forward base-transit time accounting for the base charging diffusion capacitance.
 
## Maximum Cut-Off Frequency Short-Circuit Operation




- Generally the value for the  $C_{\pi}$  is not given on BJT device data sheets, rather an alternative parameter is listed called the cutoff frequency,  $f_T$ .
- The cutoff frequency is derived from the short-circuit model of device behavior shown above.
 
## Maximum Cut-Off Frequency Frequency Analysis



$$h_{fe} \equiv \frac{I_c}{I_b} \cong \frac{g_m r_\pi}{1 + s(C_\pi + C_\mu)r_\pi} = \frac{\beta_0}{1 + s(C_\pi + C_\mu)r_\pi}$$

According to one-pole model:

 

$$\omega_\beta = \frac{1}{(C_\pi + C_\mu)r_\pi}$$

$$\omega_T = \beta_0 \omega_\beta = \frac{g_m}{C_\pi + C_\mu}$$

$C_\pi$  and  $r_\pi$  parameters  
are dependent on  
current level!

## Deriving Device Capacitance From $f_T$

$$\therefore f_T = \frac{1}{2\pi} \frac{g_m}{C_\pi + C_\mu}$$

- Given the device  $f_T$ , we can state that the sum of the internal capacitance are given by

$$\therefore C_\pi + C_\mu = \frac{1}{2\pi} \frac{g_m}{f_T}$$

- But we also know that


$$C_\pi \approx 2C_{je0} + \tau_F \frac{I_C}{V_T}$$

- Hence, we can state  $C_\mu$  as

$$\therefore C_\mu = \frac{1}{2\pi} \frac{g_m}{f_T} - C_\pi = \frac{1}{2\pi} \frac{g_m}{f_T} - \left( 2C_{je0} + \tau_F \frac{I_C}{V_T} \right)$$



## $f_T$ Frequency Dependence

 


- Parasitic capacitances,  $r_{\pi}$ , as well as  $\beta$ , depend on bias levels, hence  $f_T$  varies with bias levels.
- Lumped hybrid-p model is valid only to  $\sim 0.2 f_T$ , above this a distributed model is required.

## Outline

- Device Structure and Physical Operation
  - Current-Voltage Characteristics
- The BJT as an Amplifier
  - Biasing in BJT Amplifier Circuits
  - Small-Signal Operation and Models
- Single-Stage BJT Amplifiers
- Design Of Single-Stage BJT Amplifiers
  - Simulating BJT Circuits With SPICE
  - CE Amplifier Example
- Frequency Response Behavior
  - ➡ CE Amplifier
- Summary
 
## CE Amplifier Low Frequency Response

- The low-frequency frequency behavior is computed by ignoring the internal transistor capacitances (open circuit) and computing the transfer function of the circuit.
- Complicated transfer function analysis, instead make use of the method of **Short-Circuit Time-Constant Method**.



## Individual Time Constants Associated With $C_{C1}$ , $C_{C2}$ and $C_E$

By inspection:

$$R_{1,eq} = R_{sig} + R_B || r_\pi$$

$$\tau_1 = R_{1,eq} C_{C1} = (R_{sig} + R_B || r_\pi) C_{C1}$$

$$R_{2,eq} = R_C + R_L$$


$$\tau_2 = R_{2,eq} C_{C2} = (R_C + R_L) C_{C2}$$

$$R_{3,eq} = r_e + \frac{R_B || R_{sig}}{\beta + 1}$$



$$\tau_3 = R_{3,eq} C_E = \left( r_e + \frac{R_B || R_{sig}}{\beta + 1} \right) C_E$$

$f_L$  estimation:

$$\omega_L \cong \sum_i \frac{1}{\tau_i} = \frac{1}{(R_{sig} + R_B || r_\pi) C_{C1}} + \frac{1}{(R_C + R_L) C_{C2}} + \frac{1}{\left( r_e + \frac{R_B || R_{sig}}{\beta + 1} \right) C_E}$$

 


## CE Amplifier High-Frequency Response

  

**High-Frequency Equivalent Circuit**  
(by-pass capacitors act as shorts)

- The most direct method is to derive the transfer function of the circuit.
  - Typically a very complicated process and leads to complicated expression.
  - Make use of the method of **open-circuit time constants**.

## CE Amplifier High-Frequency Response

 

- A simplified high-frequency analysis leads to the 3-dB frequency estimate

$$f_H \approx \frac{1}{2\pi C_{in} R'_{sig}} = \frac{1}{2\pi [C_{\pi} + C_{\mu} (1 + g_m R'_L)] [r_{\pi} \parallel (r_x + R_B \parallel R_{sig})]}$$

## Summary

- The BJT is a versatile device that has been around since the late forties.
- Amplification is one of the main applications of this technology; digital logic is another.
- We learned about the nonlinear i-v characteristics of the BJT, how to analyze them in circuits.
- Due to the non-linear behavior, circuit analysis is very complicated and usually needs numerical methods to solve.
- A graphical method was introduced to aid visualization of solution space.
- An approximation method based on Taylor series approximation was introduced:
  - linear small-signal equivalent transistor model
- Linear circuit behavior such as low, mid-band and high-frequency response, was described.